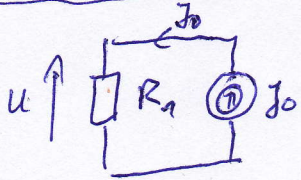


# Kolokwium 2, zadanie 2 grupa B


## Analiza dla $\omega = 0$ 1 pkt



$$P_1^{(0)} = U \cdot J_0 = J_0^2 \cdot R = 8 \text{ mW}$$

W gałęzi z  $R_2$  znajduje się pojemność i jest równoważona dla składowej stałej, zatem  $P_2^{(0)} = 0$

## Analiza dla $\omega = \omega_0$ 3 pkt

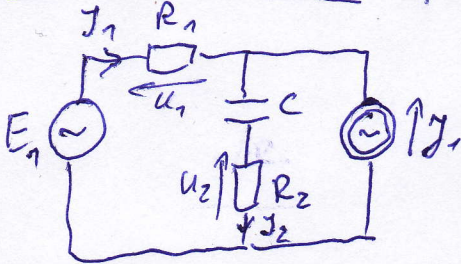

$$P_1^{(1)} = \frac{1}{2} \operatorname{Re} \{ U_1 \cdot J_1^* \} = \frac{1}{2} |J_1|^2 \cdot R_1$$

$$P_2^{(1)} = \frac{1}{2} \operatorname{Re} \{ U_2 \cdot J_2^* \} = \frac{1}{2} |J_2|^2 \cdot R_2$$

$$\begin{cases} J_2 = J_1 + J_1 \\ E_1 = J_1 R_1 + J_2 \left( \frac{1}{j\omega C} + R_2 \right) \end{cases}$$

$$E_1 = J_1 R_1 + (J_1 + J_1) \left( \frac{1}{j\omega C} + R_2 \right) \Rightarrow J_1 = \frac{E_1 - J_1 (R_2 + \frac{1}{j\omega C})}{R_1 + R_2 + \frac{1}{j\omega C}}$$

$$J_1 = \frac{4 - 4 \cdot 10^{-3} \left( 500 + \frac{1}{j 10^6 \cdot 10^{-9}} \right)}{1000 + \frac{1}{j 10^6 \cdot 10^{-3}}} = \frac{2 + j4}{1 + j} \text{ mA} = \frac{8 + j2}{2} \text{ mA} = 4 + j1 \text{ mA}$$


$$|J_1| = \sqrt{17} \text{ mA}$$

$$J_2 = J_1 + J_1 = 4 + j1 + 4 = (8 + j1) \text{ mA} \quad |J_2| = \sqrt{65}$$

$$P_1^{(1)} = \frac{1}{2} |J_1|^2 \cdot R_1 = \frac{1}{2} \cdot 17 \cdot 500 \text{ } \mu\text{W} = 4,25 \text{ mW}$$

$$P_2^{(1)} = \frac{1}{2} \cdot 65 \cdot 500 = 16,25 \text{ mW}$$
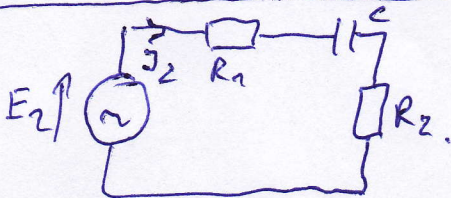
## Analiza dla $\omega = 2\omega_0$ 3 pkt



$$P_2^{(2)} = \frac{1}{2} |J_2|^2 \cdot R_2 = P_1^{(2)} \text{ gdyż } R_1 = R_2$$

$$J_2 = \frac{E_2}{R_1 + R_2 + \frac{1}{j2\omega_0 C}} = \frac{10}{1000 + \frac{1}{j2 \cdot 10^6 \cdot 10^{-9}}} = \frac{10}{1000 + j500} = \frac{20}{2 + j} \cdot 10^{-3} = \frac{40 + j20}{5} \cdot 10^{-3} =$$

$$= 8 + j4 \text{ mA}$$

$$|J_2| = \sqrt{64 + 16} = \sqrt{80}$$

$$P_1^{(2)} = P_2^{(2)} = \frac{1}{2} \cdot 80 \cdot 500 \text{ } \mu\text{W} = 20 \text{ mW}$$

Odp:

$$P_1 = 8 \text{ mW} + 4,25 \text{ mW} + 20 \text{ mW} = 32,25 \text{ mW}$$

$$P_2 = 16,25 \text{ mW} + 20 \text{ mW} = 36,25 \text{ mW}$$