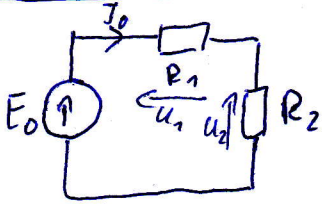


Kolokwium 2, zadanie 2, grupa C

Rozwiązanie:

Analiza dla $\omega = 0$




$$R = R_1 = R_2$$

$$u_1 = u_2 = \frac{E_0}{2}$$

$$P_1^{(0)} = P_2^{(0)} = u_1 \cdot J_0 = u_2 \cdot J_0 = \frac{u_1^2}{R} = \frac{E_0^2}{4R} = \frac{64}{4 \cdot 2 \cdot 10^3} = \underline{\underline{8 \text{ mW}}}$$

Analiza dla $\omega = \omega_0$

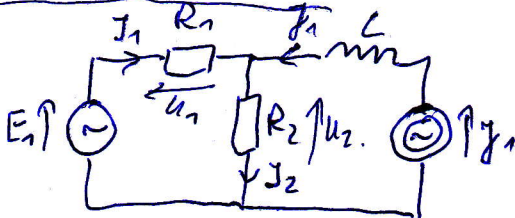

$$J_2 = J_1 + y_1$$

$$E_1 = J_1 R_1 + J_2 R_2$$

$$E_1 = J_1 R_1 + J_1 R_2 + J_1 R_2 \Rightarrow J_1 = \frac{E_1 - J_1 R_2}{R_1 + R_2} = \frac{4 - 2 \cdot 10^3 \cdot 4 \cdot 10^{-3}}{4 \cdot 10^3} = \frac{-4}{4} \cdot 10^{-3} = -1 \text{ mA}$$


$$J_2 = -1 \text{ mA} + 4 \text{ mA} = 3 \text{ mA}$$

$$|J_1| = 1 \text{ mA} \quad |J_2| = 3 \text{ mA}$$

$$P_1^{(1)} = \frac{1}{2} \operatorname{Re} \{ J_1 \cdot u_1^* \} = \frac{1}{2} |J_1|^2 \cdot R_1 = \frac{1}{2} \cdot 10^{-6} \cdot 2 \cdot 10^3 = \underline{\underline{1 \text{ mW}}}$$

$$P_2^{(2)} = \frac{1}{2} \operatorname{Re} \{ u_2 \cdot J_2^* \} = \frac{1}{2} |J_2|^2 \cdot R_2 = \frac{1}{2} \cdot 9 \cdot 10^{-6} \cdot 2 \cdot 10^3 = \underline{\underline{9 \text{ mW}}}$$

Analiza dla $\omega = 2\omega_0$

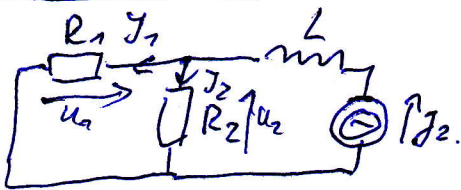

$$u_1 = u_2 \quad J_1 = J_2 = \frac{y_2}{2}$$

$$P_1^{(2)} = P_2^{(2)} - \text{gdzie } R_1 = R_2 \text{ i } J_1 = J_2$$

$$P_1^{(2)} = P_2^{(2)} = \frac{1}{2} |J_1|^2 \cdot R = \frac{1}{2} \cdot \frac{y_2^2}{4} \cdot R = \frac{1}{8} \cdot 4 \cdot 10^{-6} \cdot 2 \cdot 10^3 = \underline{\underline{1 \text{ mW}}}$$

$$P_1 = P_1^{(0)} + P_1^{(1)} + P_1^{(2)} = 8 \text{ mW} + 1 \text{ mW} + 1 \text{ mW} = \underline{\underline{10 \text{ mW}}}$$

$$P_2 = P_2^{(0)} + P_2^{(2)} + P_2^{(2)} = 8 \text{ mW} + 9 \text{ mW} + 1 \text{ mW} = \underline{\underline{18 \text{ mW}}}$$